

# Seven Segment Display through AVR-Assembly



1

## G V V Sharma\*

#### **CONTENTS**

## 1 Components

## 2 Controlling the Display

Abstract—The objective of this manual is to show how to control a seven segment display through the AVR-Assembly.

#### 1 Components

Component	Value	Quantity	
Breadboard		1	
Resistor	$\geq 220\Omega$	1	
Arduino	Uno	1	
Seven Segment	Common	1	
Display	Anode		
Jumper Wires		20	

TABLE 0

#### 2 Controlling the Display

1. Complete Table 1 for all the digital pins using Fig. 1.


Port Pin	Digital Pin		
PD2	2		
PB5	13		

TABLE 1

2. Make connections according to Table 2.

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

### Atmega168 Pin Mapping

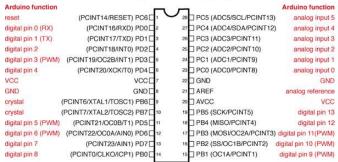

Digital Pins 11,12 & 13 are used by the ICSP header for MOSI, MISO, SCK connections (Almega168 pins 17,18 & 19). Avoid low-impedance loads on these pins when using the ICSP header.

Fig. 1

A 1 ·	2	3	4	5	6	7	8
Arduino	PD2	PD3	PD4	PD5	PD6	PD7	PB0
Display	a	b	С	d	e	f	g
2	0	0	1	0	0	1	0

TABLE 2

3. Execute the following code. The number 2 should be displayed.

wget https://raw.githubusercontent.com/gadepall/arduino/master/assembly/sevenseg/codes/sevenseg.asm

4. Now generate the numbers 0-9 by modifying the above program.