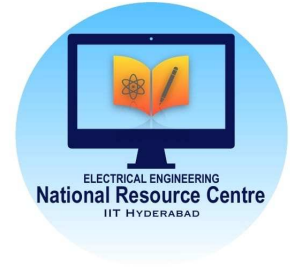




Karnaugh Map with Dont Care Conditions



G V V Sharma*

CONTENTS

1 Don't Care Conditions

References

Abstract—This manual explains Karnaugh maps (K-map) using don't care conditions.

1 DON'T CARE CONDITIONS

1. Don't Care Conditions: 4 binary digits are used in the incrementing decoder [1]. However, only the numbers from 0-9 are used as input/output in the decoder and we *don't care* about the numbers from 10-15. This phenomenon can be addressed by revising the truth table in [1] to obtain Table 1.
2. The revised K-map for A is available in Fig. 2. Show that

$$A = W' \quad (1.1)$$

3. The revised K-map for B is available in Fig. 3. Show that

$$B = WX'Z' + W'X \quad (1.2)$$

4. The revised K-map for C is available in Fig. 4. Show that

$$C = X'Y + W'Y + WXY' \quad (1.3)$$

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	-	-	-	-
1	0	1	1	-	-	-	-
1	1	0	0	-	-	-	-
1	1	0	1	-	-	-	-
1	1	1	0	-	-	-	-
1	1	1	1	-	-	-	-

TABLE 1

5. The revised K-map for D is available in Fig. 5. Show that

$$D = W'Z + WXY \quad (1.4)$$

6. Verify the incrementing decoder with don't care conditions using the arduino.
7. Display Decoder: Use K-maps to obtain the minimized expressions for a, b, c, d, e, f, g in terms of A, B, C, D with don't care conditions.
8. Verify the display decoder with don't care conditions using arduino.

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

ZY \ XW	00	01	11	10
00		0	0	
01		0	0	
11	-	-	-	-
10		0	-	-

Fig. 2: K-map for A with don't cares.

ZY \ XW	00	01	11	10
00	0	0		0
01			0	
11	-	-	-	-
10	0	0	-	-

Fig. 4: K-map for C with don't cares.

ZY \ XW	00	01	11	10
00	0		0	
01	0		0	
11	-	-	-	-
10	0	0	-	-

Fig. 3: K-map for B with don't cares.

ZY \ XW	00	01	11	10
00	0	0	0	0
01	0	0		0
11	-	-	-	-
10		0	-	-

Fig. 5: K-map for D with don't cares.

REFERENCES

- [1] G. V. V. Sharma. Karnaugh Map. [Online]. Available: https://github.com/gadepall/arduino/raw/master/ide/kmap/gvv_kmap.pdf